
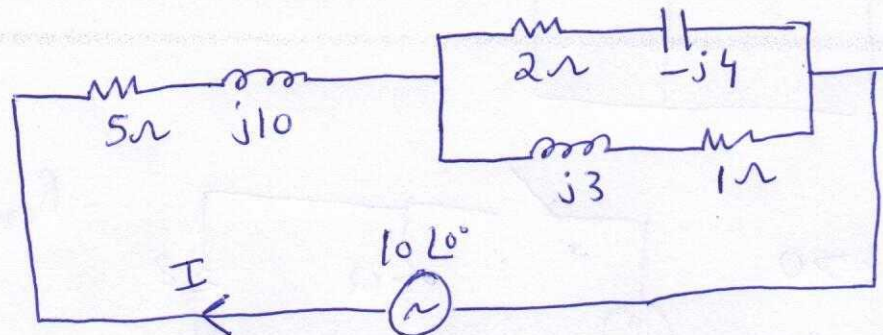


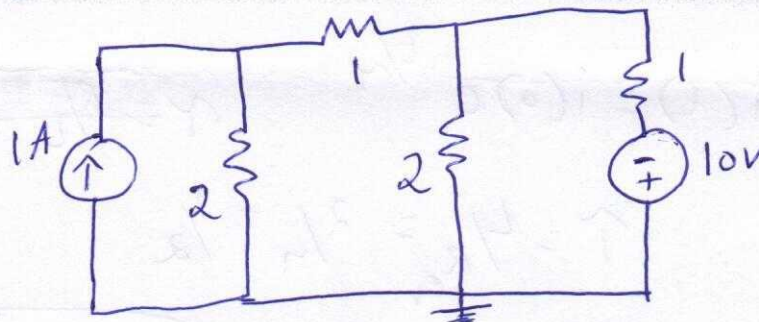
1. For the given circuit, find I and power factor
(5 marks)



2. Using mesh analysis, find the current
(4 Marks) through 10V source



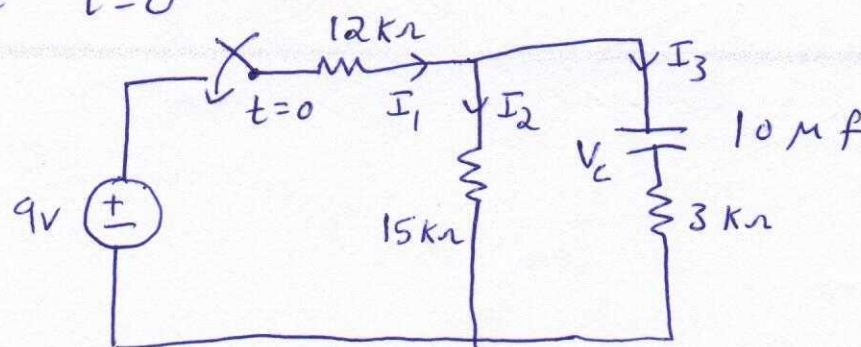3. for the given circuit. Find I_1, I_2, I_3 & V_C
at $t=0$
(4 Marks)



4) find $i(t)$ for $t > 0$. switch open at $t = 0$

