

Basic Electronics Circuit's Lab

Experiment no. 4

1. Characteristics of BJT transistor in Common Emitter Configuration

The basic circuit diagram for studying characteristics of BJT is shown in the Fig. 1.1. The input voltage is applied between base and emitter terminals and the output voltage is measured between collector and emitter terminals. Here emitter region of the transistor is common to both input and output and hence the name common emitter configuration. While performing the experiment do not exceed the ratings of the transistor. This may lead to damage the transistor. Connect voltmeter and ammeter or multi meters with correct polarities as shown in the circuit diagram.

Input characteristics are obtained between the input current (I_B) and input voltage (V_{BE}) by keeping the output voltage (V_{CE}) constant.

Procedure:

1. Connect the circuit as shown in Fig 1.1
2. Keep output voltage $V_{CE} = 0$ V by varying V_{CC} .
3. Varying V_{BB} gradually, note down base current I_B and base-emitter voltage V_{BE} .
4. Vary in steps of 0.2 V from 0 V to 1 and in steps of 1 V from 1 to 12 V.
5. Repeat above procedure (step 3) for $V_{CE} = 5$ V. Tabulate readings in Table 1.1
6. Plot the graph between V_{BE} and I_B for constant V_{CE} values as in Graph 1.1.

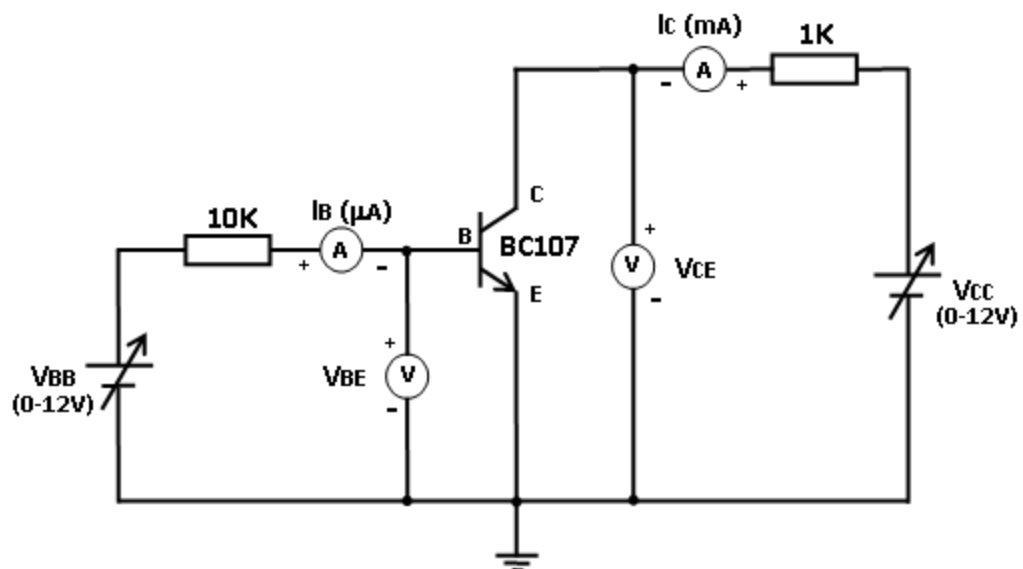


Fig. 1.1: Circuit for plotting input characteristics of BJT in CE configuration


V _{CE} = 0 V		V _{CE} = 5 V	
I _B (μA)	V _{BE}	I _B (μA)	V _{BE}

Table. 1.1

To obtain input resistance find V_{BE} and I_B for a constant V_{CE} on one of the input characteristics.

Input Resistance $h_{ie} = r_i = \frac{\Delta V_{BE}}{\Delta I_B} \quad (V_{CE} \text{ Constant})$ -----

Reverse Voltage Gain $h_{re} = \frac{\Delta V_{BE}}{\Delta V_{CE}} \quad (I_B \text{ Constant})$ -----

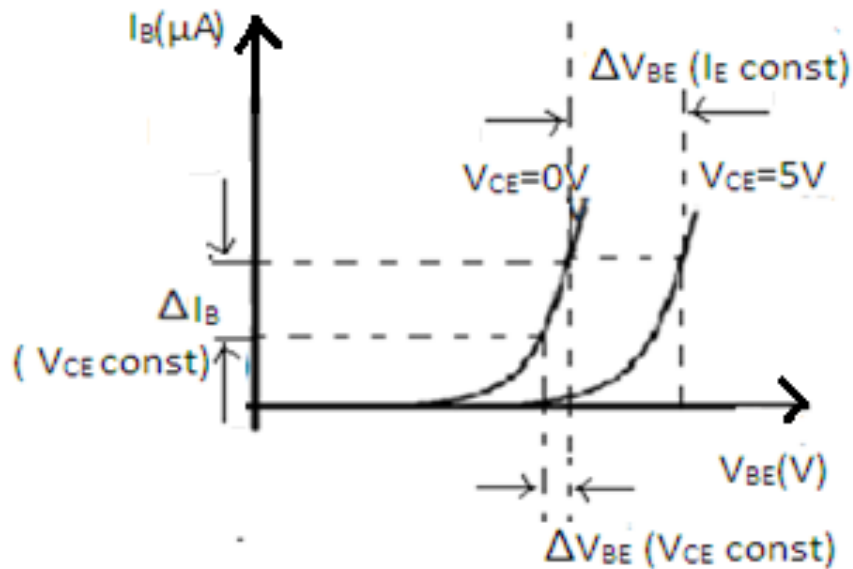

Graph 1.1: Input characteristics of BJT in CE configuration

Output characteristics are plotted between the output voltage (V_{CE}) and output current (I_C) at constant input current (I_B).

1. Connect the circuit as shown in the Fig 1.2.
2. Keep base current $I_B = 10 \mu A$ by varying V_{BB} .
3. Varying V_{CC} gradually in steps of 1V up to 15V and note down collector current I_C and Collector-Emitter Voltage (V_{CE}).
4. Repeat above procedure (step 3) for $I_B = 20 \mu A$, $30 \mu A$ and $40 \mu A$. Tabulate readings in Table 1.2.
5. Plot the graph between V_{CE} and I_C for different values of I_B as in graph 1.2


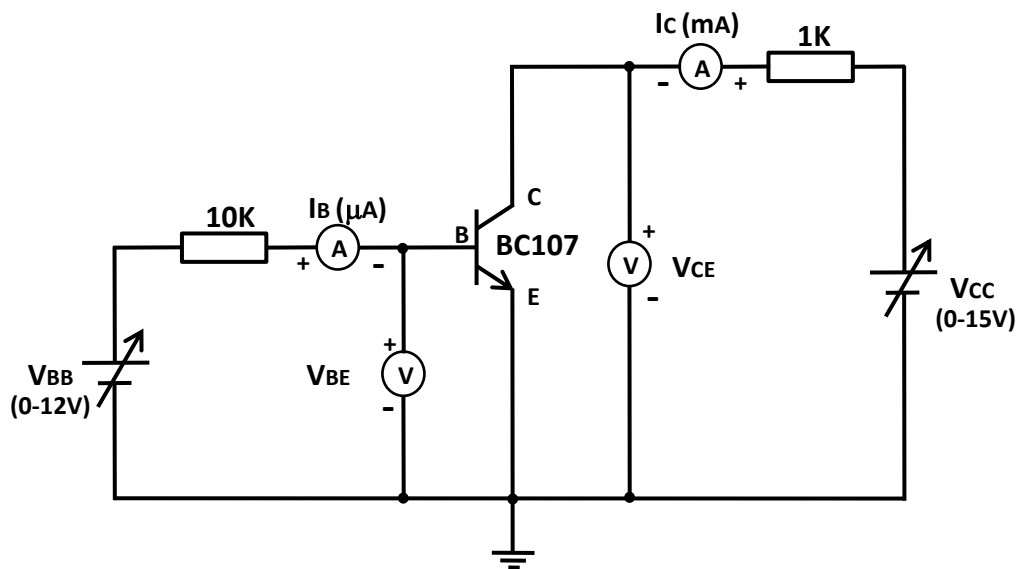


Fig. 1.2: Circuit for plotting output characteristics of BJT in CE configuration

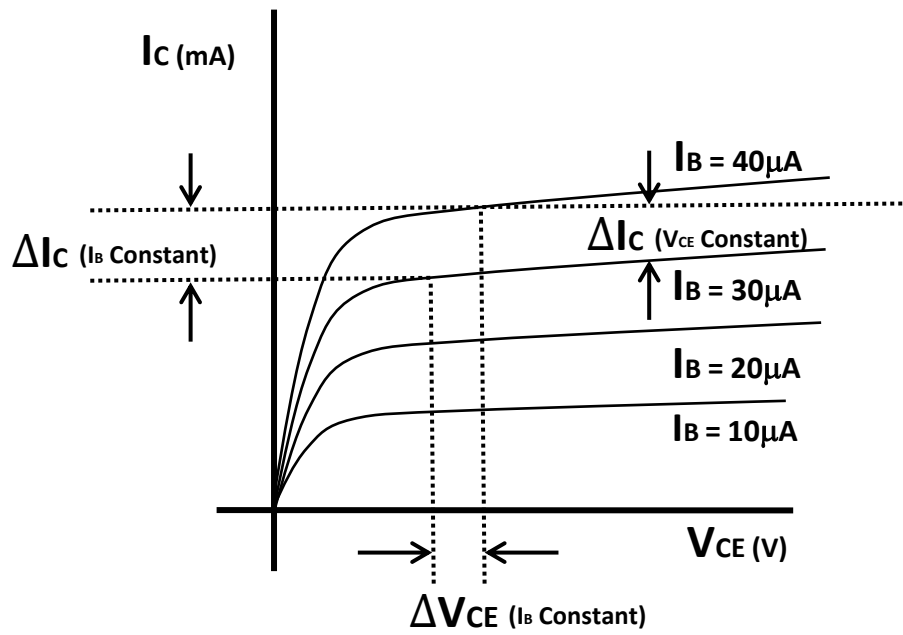

Graph 1.2: Output characteristics of BJT in CE configuration