

Assignment : Due date Oct 9<sup>th</sup>, 6PM.

Late and plagiarized submissions will be penalized

1) For an series RLC circuit, given the KVL expression 
$$L \frac{di(t)}{dt} + Ri(t) + v_c(t) = V_s$$

where  $V_s$  is the voltage source that is connected to RLC circuit.

In the above expression substitute  $i(t) = C \frac{dv_c(t)}{dt}$  and obtain the second order differential equation in terms of  $V_c$ . For the same differential equation derived in terms of  $V_c$

- Obtain the complete solution.
- Assuming  $V_s$  is disconnected from the circuit, obtain the natural or transient solution for i) Underdamped ii) overdamped and iii) Critically damped
- Draw the  $V_c$ -t curves for each case mentioned in (b).
- compare the  $V_c(t)$ -t curves and  $i(t)$ -t curves for the series RLC circuit for each case mentioned in (b) and comment on the nature of the curves
- comment on the Value of  $V_c(t)$  and  $i(t)$  at  $t=0$  and  $t=\infty$ .

2) A  $15\mu\text{F}$  capacitor is connected in series with a  $1.1\text{M}\Omega$  resistor. This series combination is connected across a 120V dc supply. Calculate


- The time constant of the circuit
- The initial value of the charging current
- The initial rate of rise of voltage across the capacitor
- The voltage across the capacitor after a time equal to the time constant.
- The circuit current after a time equal to the time constant
- The voltage across capacitor at 4 seconds after switch on.
- the time taken by the capacitor voltage to reach 60V.

3) A 160V source is connected in series to  $25\mu\text{F}$  capacitor and a  $90\text{K}\Omega$  resistor. Calculate

- The time constant of the circuit and ii) steady state current

The source is disconnected when the capacitor is fully charged and a  $5\mu\text{F}$  capacitor is connected in parallel with the  $25\mu\text{F}$  capacitor. Assume that there is no loss of charge in the process. The combination is discharged through the  $(90+10)\text{K}\Omega$  resistor. How long from the commencement of discharge will the voltage take to fall to 40V.

4) Find  $V_o(t)$  from the circuit

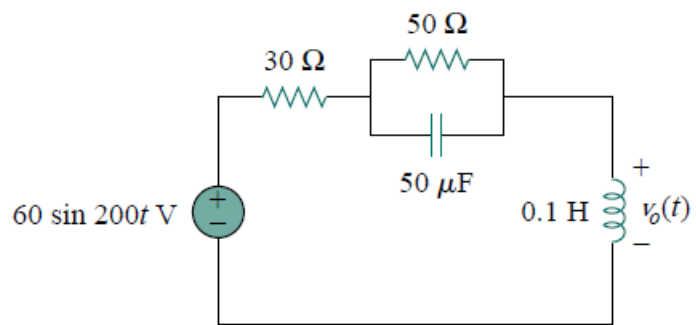

5) If the source frequency is 60Hz. Find  $i_1(t)$  and  $i_2(t)$ .

