


# Basic Electronics Circuit's Lab

## Experiment no. 5

### 1. Design of Operational Amplifier Configurations

- a) Inverting Amplifier
- b) Non - Inverting Amplifier
- c) Summing Amplifier
- d) Differential Amplifier
- e) Instrumentation Amplifier.

The pin diagram for op-amp 741 is shown in Fig. 5.1. The circuit configurations for inverting amplifier, non-inverting amplifier, summing amplifier, differential amplifier and instrumentation amplifier are shown in Figs 5.2 to 5.6.

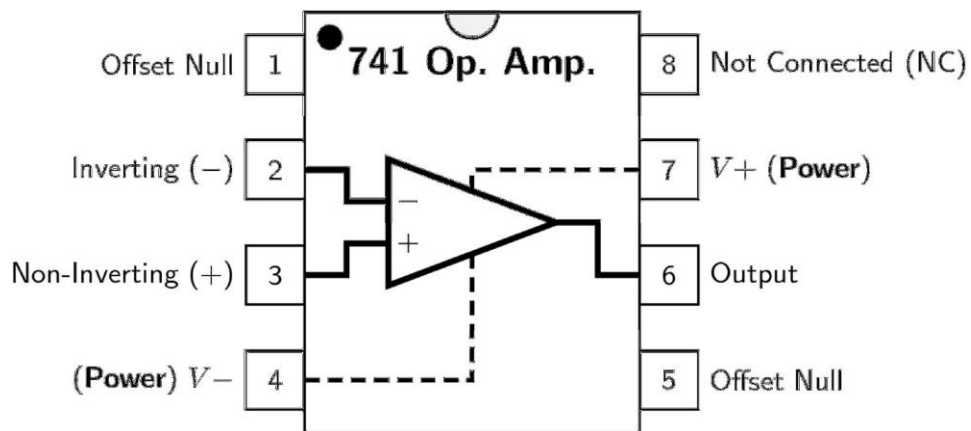

**Fig. 5.1: Pin diagram for 741 op-amp**

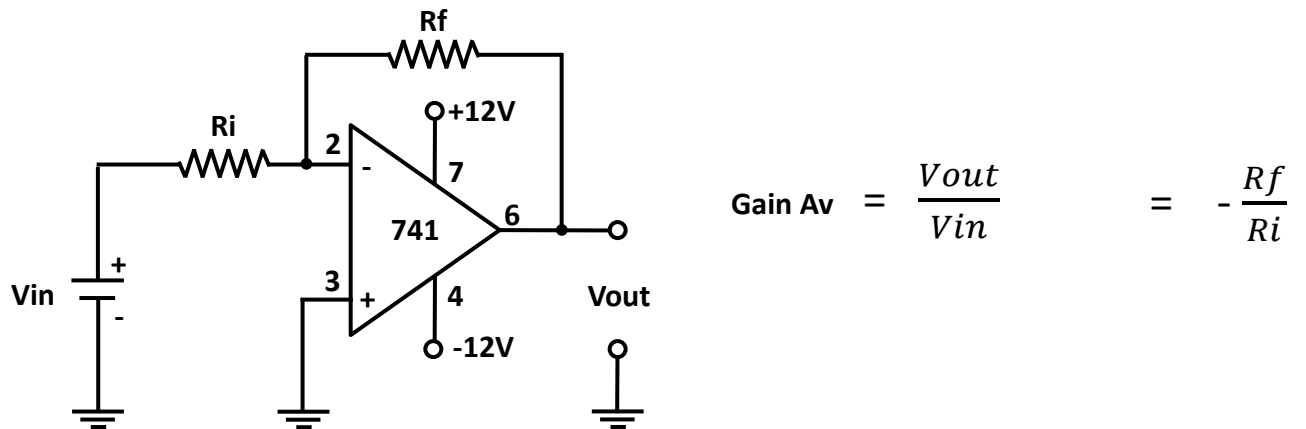


Fig.5.2: Inverting Amplifier

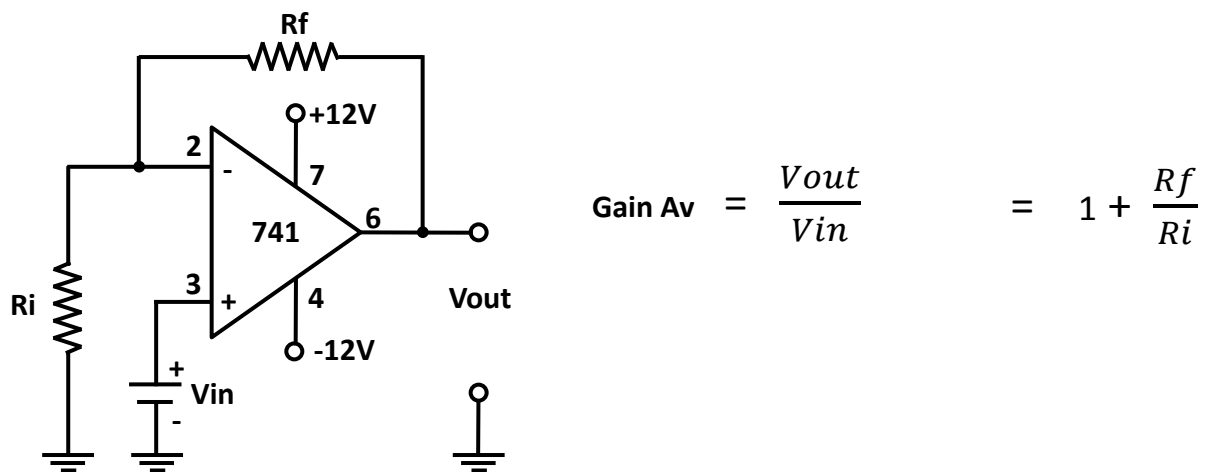


Fig. 5.3: Non-inverting Amplifier

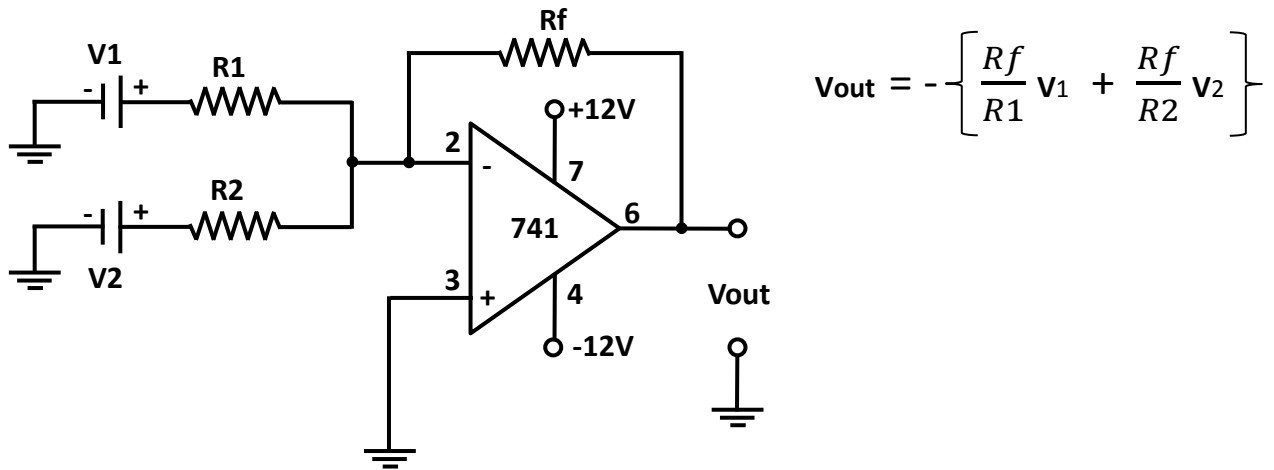


Fig. 5.4: Summing Amplifier


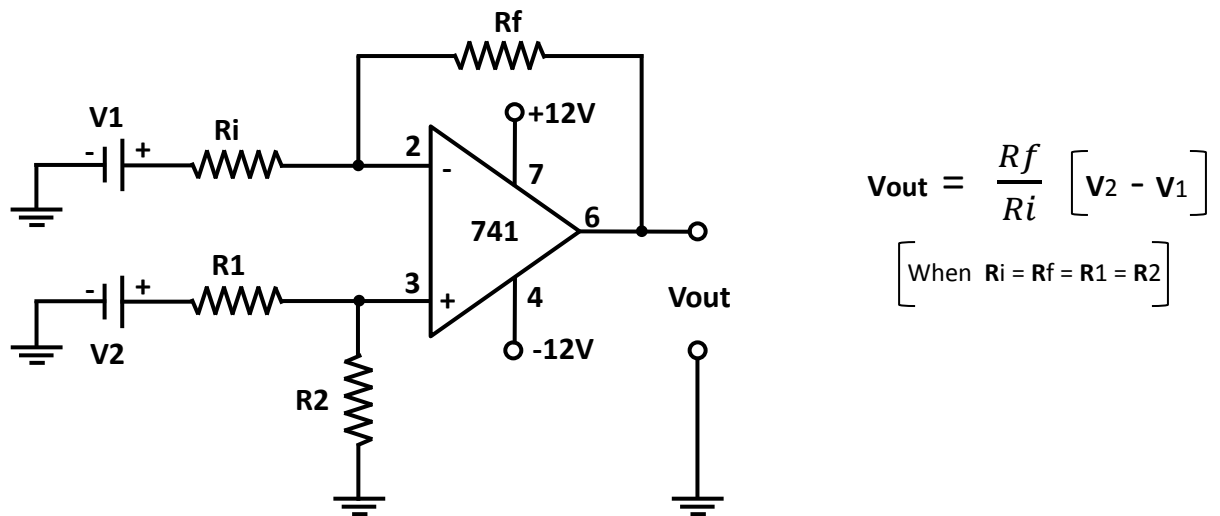


Fig. 5.5: Differential Amplifier

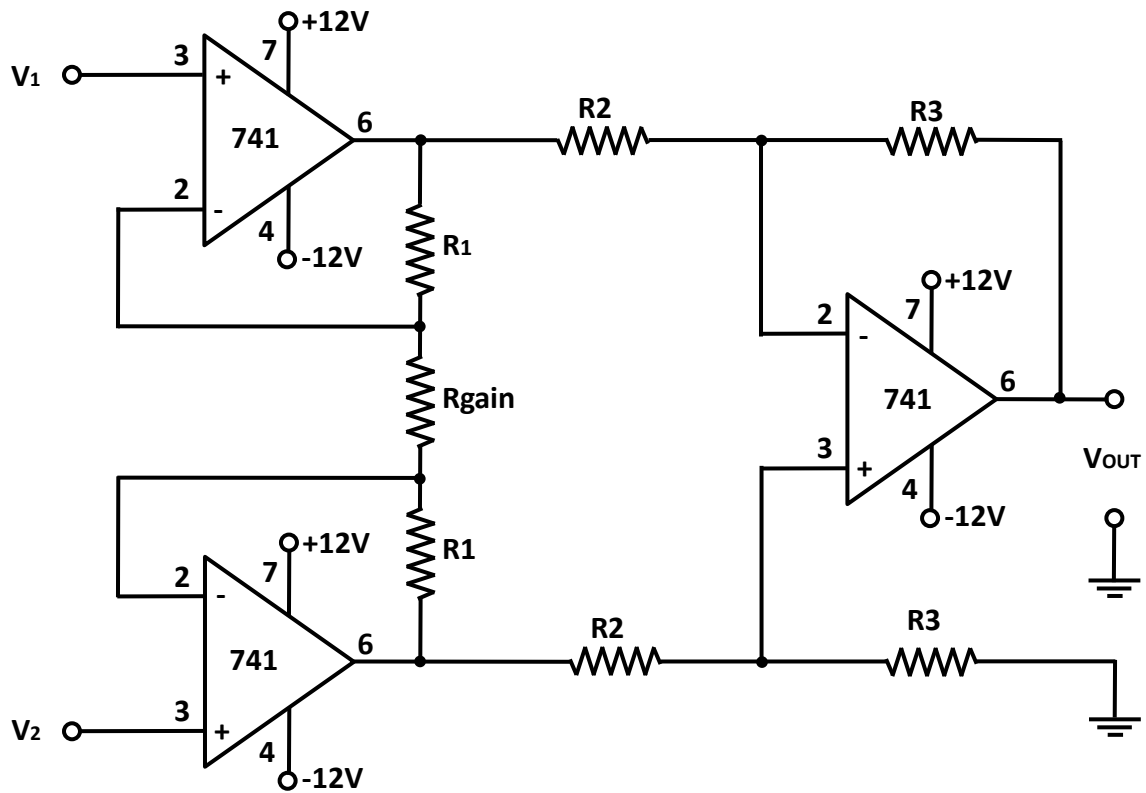

$$\text{Gain } A_v = \frac{V_{out}}{V_2 - V_1} = \left( 1 + \frac{2R_1}{R_{gain}} \right) \frac{R_3}{R_2}$$

**Fig. 5.6: Instrumentation amplifier**

**Note:** Apply ac inputs from function generator and observe the wave forms and plot them.